Hardware Setup:

I started with the basic breadboard setup that was covered.

Ground Connections:

There is a small resistor located towards the bottom of the board, connected from a63 to negative. That rail allows for the other resistors to be connected to the negative rail.

Button:

The button is read on GPIO 15, read with Pin.IN, PULL_DOWN, button.value() == 1 means that the button has been pressed.

Two wires connect the button circuit

- Row 61i -> negative (ground) rail at row 57
- Row 63c -> row b20, which lines up with the Pico's GPIO 15 leg

LEDs:

All 5 LEDs have two legs, a long leg and a short leg. Every LED has its own resistor and its own wire. The resistor has a leg that sits next to the short leg of the LED, and the other leg is connected to the negative rail. One leg of the wire sits next to the LED's front leg, and the other leg connects to its corresponding Pico GPIO leg.

LED	Long Leg	Short Leg	Resistor	Wire to Pico
Red (GP20)	25c	27c	27a -> negative rail (row 21)	2d -> row 15j (Pico GP20)
Yellow(GP21)	25h	27h	27j -> negative rail (row 27)	25j -> row 14j (Pico GP21)
Blue(GP22)	31b	33b	33a -> negative rail (row 29)	31c -> row 15j (Pico GP16)
Green(GP16)	31i	33i	33j -> negative rail (row 30)	31j -> row 16j (Pico GP16)
White(GP17)	38d	40d	40a -> negative rail (row 37)	38e -> row 19j (Pico17)